

April 3rd (Monday)

Road map for the 2nd half of the Semester:

ITDT (Industrial IoT):

ADC Data Validation → ^① F.I.T.
(Fast Fourier Transform)
Analog Sensor interface Design.

② Power Spectrum Technique.
③ Hardware Architecture Aspects

Ion Selective Electrode Sensors
Many Applications in different Industry Sector.

the Semester.

Example: for Analog ISE Sensor interface Design.

Ref:

2018S-20-NH3- 4Design2018-1-16.pdf

ammonia/ammonium ele

Cat No. S-05722-16 model 9512BNWP

Ammonia (NH₃)
Ammonium (NH₄⁺)

1. For both drinking water and was
2. EPA-approved for ISE analysis
3. The Orion ammonia electrode is with a chemical-resistant transluce
4. The easy-to-fill electrode comes to avoid overfilling and to monitor ti
without disassembling the electro
5. Membrane replacement options loose membranes or preassembled membrane for the convenience of i
your own membrane.

20 replacement membranes, preassembled body with membrane, 60-mL of filli cable with BNC connector.

620

Fig.1

Google Definition:

Principle of ion-selective electrode (I.S.E.) An ideal I.S.E. consists of a thin membrane across which only the intended ion can be transported. The transport of ions from a high conc. to a low one through a selective binding with some sites within the membrane creates a potential difference.

Example of A Battery

Homework Extension Next Monday with Demo.

Project: Due the 2nd of the Semester.

Implementation (1/3) 330%
PID.
I₂C Sensor
PWM motor Control
Pre-processing C.F.T.
ADC

Research Part: (1/3)
① P.R.T Presentation ON State-of-the-Art Technology in the Embedded world.

② Report (Guideline)

③ Proposal (one page), Submit to the CANVAS for Approval.

— By Wednesday / Monday Next
(1/3) Demo & Presentation: By the end of

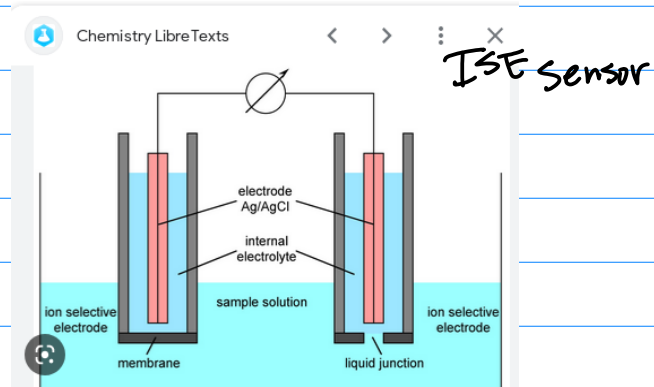


Fig.2

Working Principle of Battery - Electrical E...

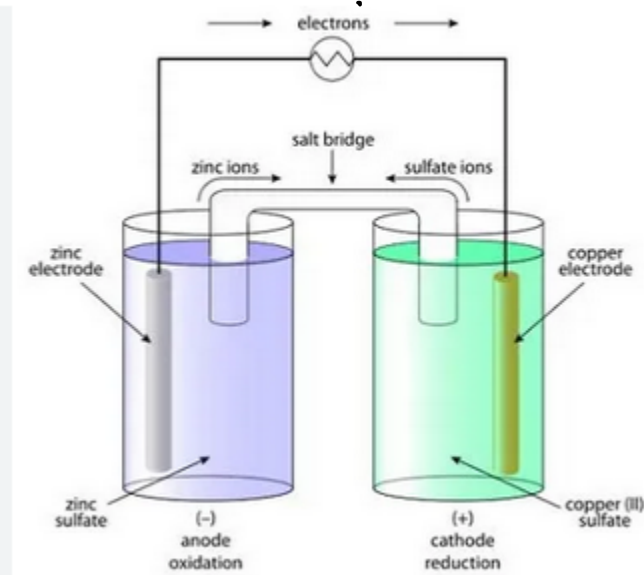


Fig. 3

Observation: Use Battery As An Example to Demonstrate Ion Selective Electrode Sensor. See $\text{NH}_3/\text{NH}_4^+$ sensor in Fig. 1.

Visit

Note 2: For the Non Linear Part, Let's perform Linearization — By using piece-wise Linear Lines.

Piece-wise Line 1.
Piece-wise Line 2.

Next step is to formulate each line by using Linear Equation.

$$\frac{y_2 - y_1}{x_2 - x_1} = \frac{y - y_1}{x - x_1} \dots (1)$$

Solve for $y = bx + c$ (see the previous Notes).

With Simplification By Removing Very Low Concentration Part, we have

Characteristic Typical NH_3 Calibration Curve

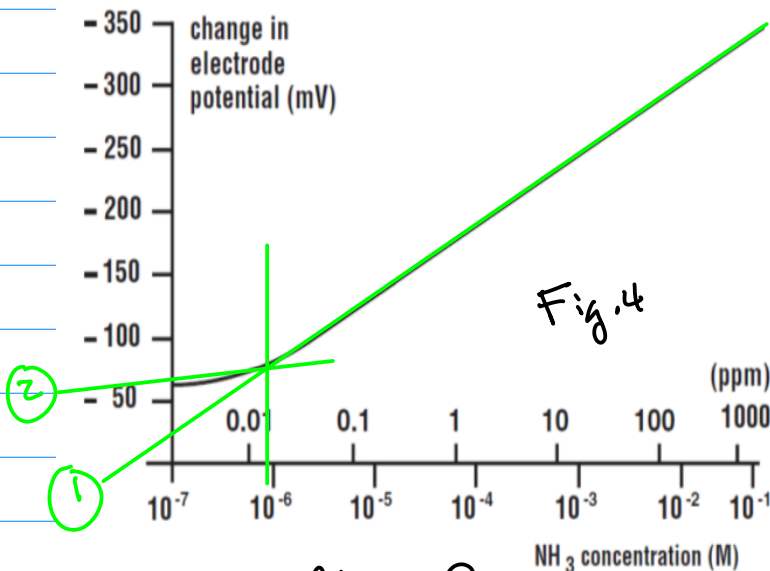


Fig. 4

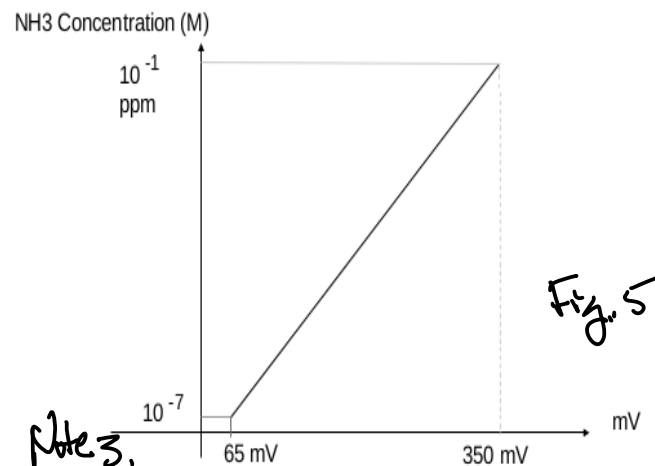


Fig. 5

Note 3.

Then, Change the Cal-Curve to the Characteristic Curve e.g. Horizontal axis is voltage for the Design of interface.

Note 1. We like to have the Linear Characteristics from the Calibration Curve. Such as $[1, 10]$, $[10, 100]$, $[100, 1000]$, etc.

Industrial Analog Sensor Interface Protocol:

- 1° Output has to be defined by Current.
- 2° The Range $4 \sim 20 \text{ mA}$.

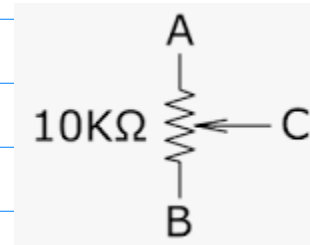


Fig. 1



Control.com

<https://control.com> > Technical Articles


Why is 4-20 mA Current Used for Industrial Analog Sensors?

Note 4. Fit to the Dynamic Range of your target platform.

External ADC Needed

CMOS Range ADC [0, 3.3]

TTL " " [0, 5.0]

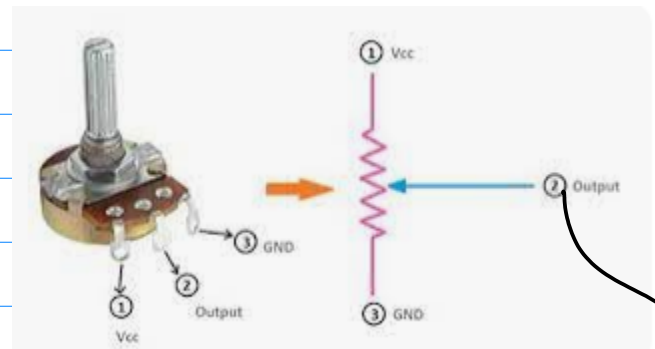

April 5th (Wed)

Note 1° New updated Due Date for the Motor Control, please use PWM from your target platform as the input to the Motor Controller.

2° ADC Unit for the project Selection Guide.

1° Interface protocol I2C; $\sim 4 \text{ Mbps}$

2° $0.5 \sim 2 \text{ MSPS}$
(Million Samples per Second)

3° $10 \sim 12 \text{ bits per Sample}$.

Example: P.O.T.

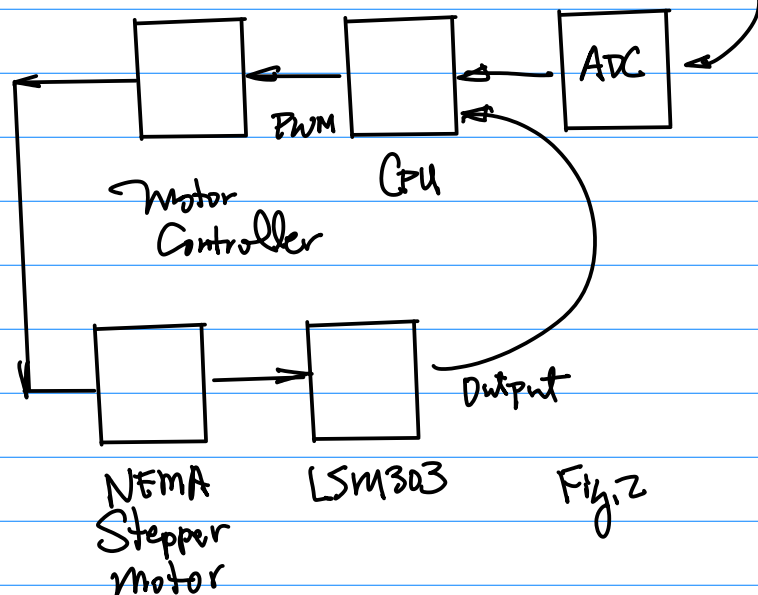


Fig. 2

<https://www.adafruit.com/product/1083>

ADS1015 12-Bit ADC - 4 Channel with Programmable Gain Amplifier - STEMMA QT / Qwiic

Product ID: 1083

\$9.95

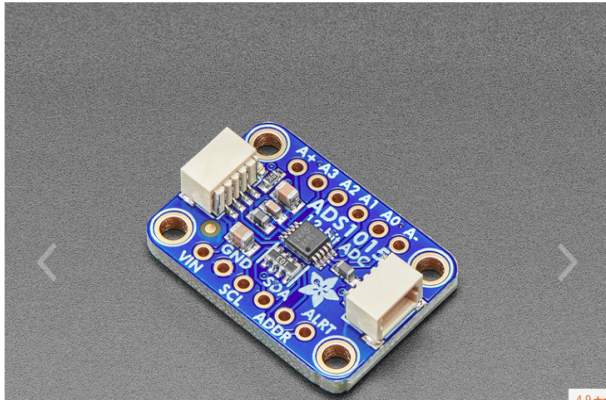


Fig.3



www.ti.com

SBAS473C –MAY 2009–REVISED OCTOBER 2009

ADS1013
ADS1014
ADS1015

Note: Input Voltage Range

ELECTRICAL CHARACTERISTICS

All specifications at -40°C to $+125^{\circ}\text{C}$, $V_{\text{DD}} = 3.3\text{V}$, and Full-Scale (FS) = $\pm 2.048\text{V}$, unless otherwise noted. Typical values are at $+25^{\circ}\text{C}$.

PARAMETER		TEST CONDITIONS	ADS1013, ADS1014, ADS1015			UNIT
			MIN	TYP	MAX	
ANALOG INPUT						
Full-scale input voltage ⁽¹⁾		$V_{IN} = (AIN_P) - (AIN_N)$		$\pm 4.096/\text{PGA}$		V
Analog input voltage		AIN_P or AIN_N to GND	GND		V_{DD}	V
Differential input impedance				See Table 2		
Common-mode input impedance		$FS = \pm 6.144V^{(1)}$		10		MΩ
		$FS = \pm 4.096V^{(1)}, \pm 2.048V$		6		MΩ
		$FS = \pm 1.024V$		3		MΩ
		$FS = \pm 0.512V, \pm 0.256V$		100		MΩ

Example: Design Objective .

1^o Selection of An ADC . 1024

Construct the Characteristic Curve of the ADC

$V_{\text{max}} = 3.3\text{V}$ for CMOS


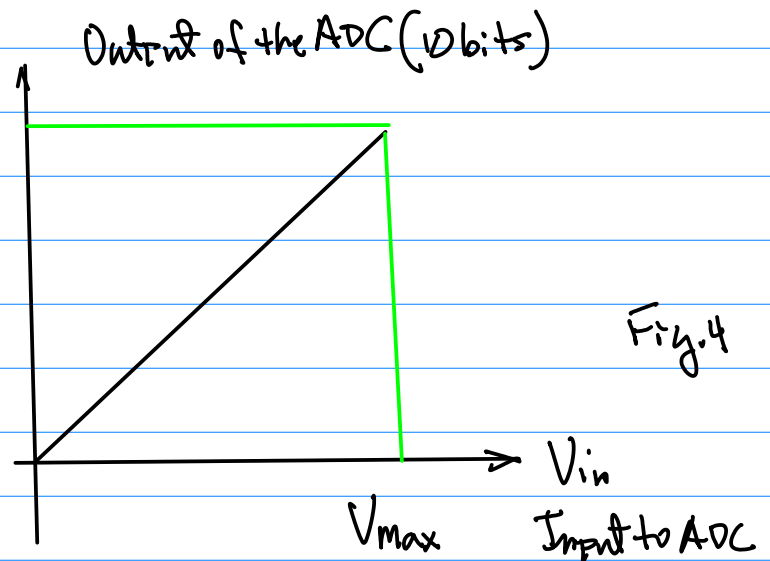
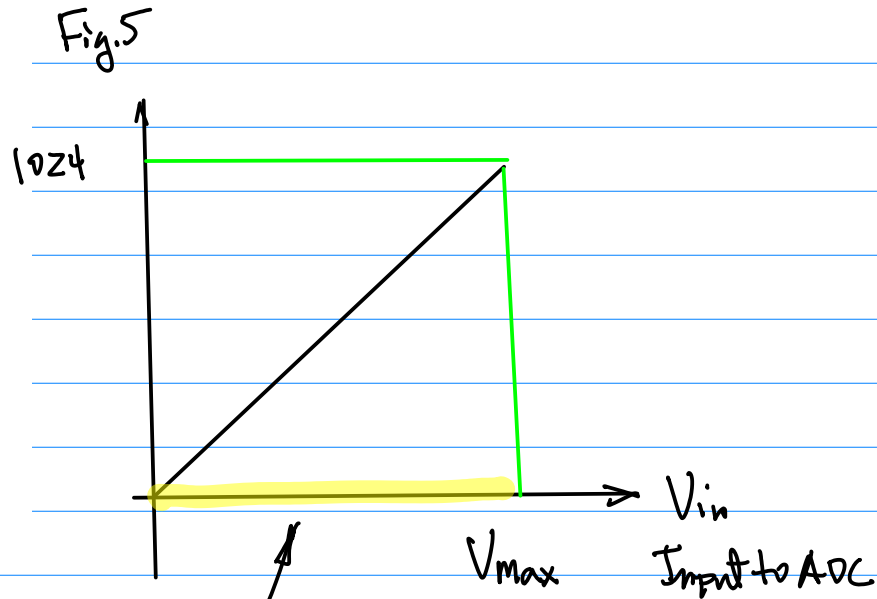


Fig.4

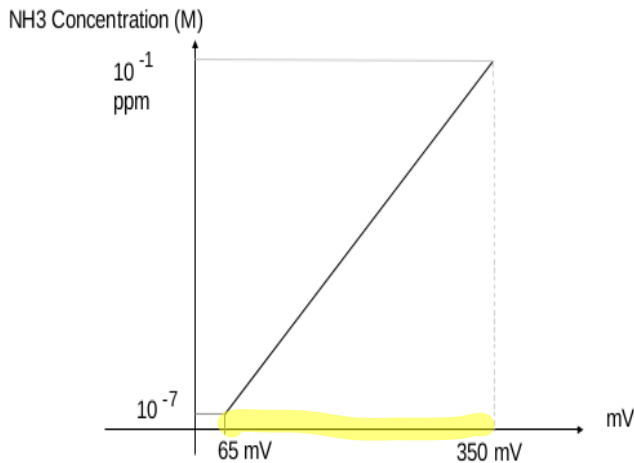2^o Design Objective: To Design
A pre-process unit to make the
Analog Sensor Output match to
the ADC input dynamic Range.



Step 1. 65 mV \rightarrow 0
350 mV \rightarrow V_{max}

In general,

$$V_{S,min} \rightarrow V_{ADC,min} \quad \dots (1)$$

$$V_{S,max} \rightarrow V_{ADC,max} \quad \dots (2)$$

At info (mon).

Example: Continuation of the
Preprocessing Design.

Note 1. Check 1015 ADC Dynamic
Range for the Input.

[0, 3.3V]. Verification is needed


Theoretical Analysis:

Step 1. Provide "offset" to shift

The Sensor dynamic Range,
Subtraction Can be utilized for
this purpose. e.g.

$$V_{sen} - V_{offset} \quad \dots (1)$$


which will lead to the Result Below.

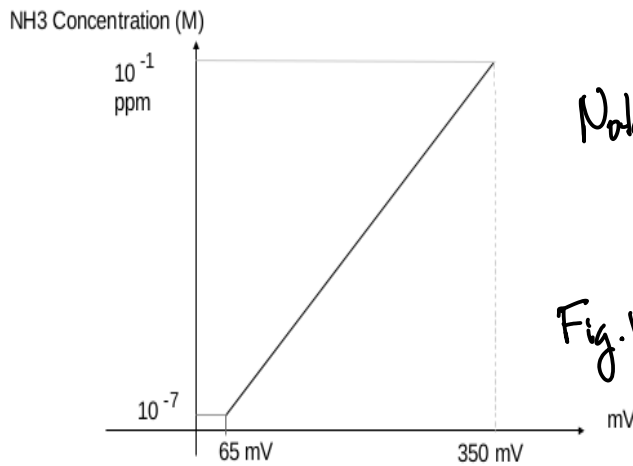


Note 1. For more generalized Case, Let $V_{min} = 65 \text{ mV}$, $V_{max} = 350 \text{ mV}$.
So, the offset $= -V_{min}$.

then, the Upper Bound after offset is

$$V_{max} - V_{min}$$

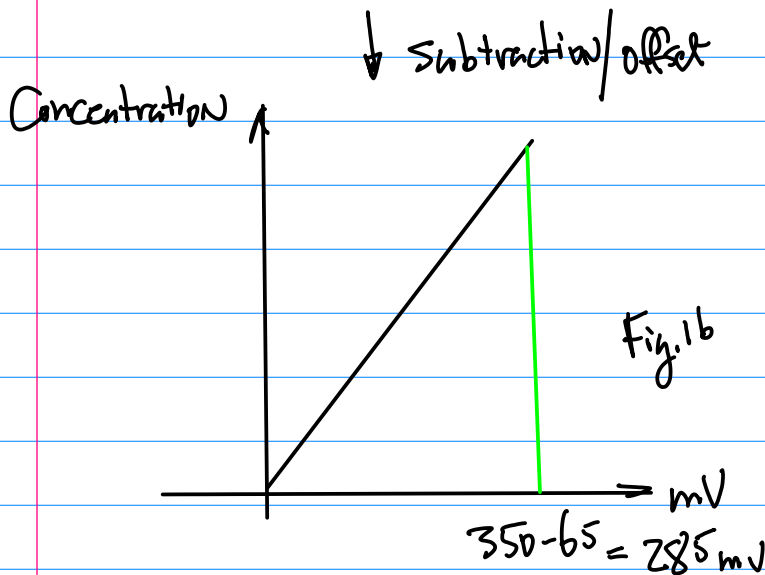

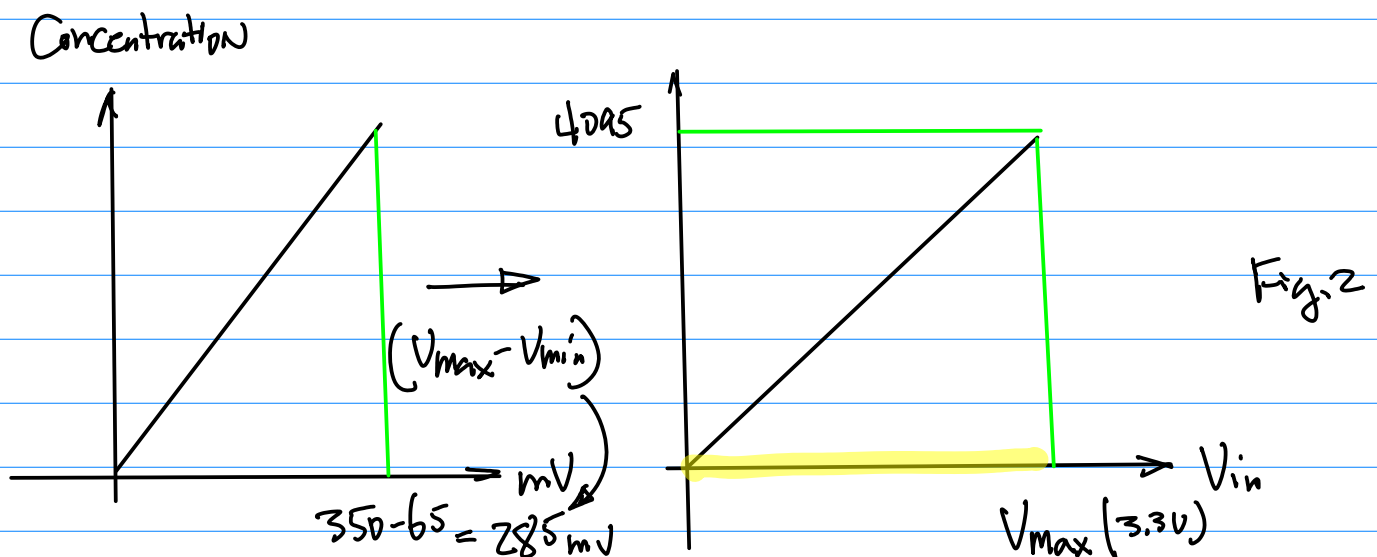Step 2. To magnify the sensor output range to match the entire Dynamic Range of the ADC.



Find the Gain for the Magnification

$$A = \frac{V_{\text{Output Range}}}{V_{\text{Input Range}}} = \frac{3.3}{285 \times 10^{-3}} \approx 11.58$$

Where 3.3 VDC is from 1015 ADC for Example.

Example: Hardware Design for the pre-processing.
Ref.


1-0Lecture 10 OpAmp Circuits.pdf

Note 1: Using OpAmp for Pre-processing
Not for the Buffering.

OpAmp Device As a Buffering Stage

Both Analog and Digital Circuit

Note 2: Background

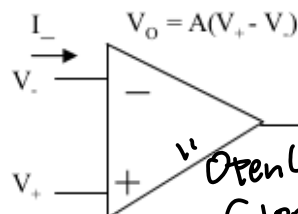


(1) To protect the previous stage's output signal, which is the input to the next stage, while sampling/connecting the signal to its next stage logic circuit. (2) Unit gain non-inverting OpAmp configuration is an excellent choice.

Ideal OpAmp Properties: (1) very large gain, $A \gg M$; (2) draws very little current, $I \sim 0$, e.g., very high impedance; (3) $V_O = A(V_+ - V_-)$ is finite range, which leads to $V_+ = V_-$.

for Example
100 MΩ or
higher.


so R_2 for feedback
 $A = 1 + \frac{R_2}{R_1}$

Harry Li, PH.D. SJSU

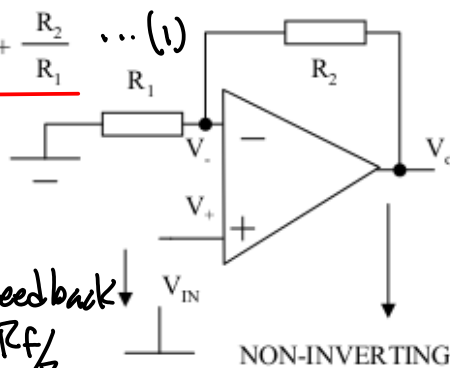

NON-INVERTING

Fig. 3

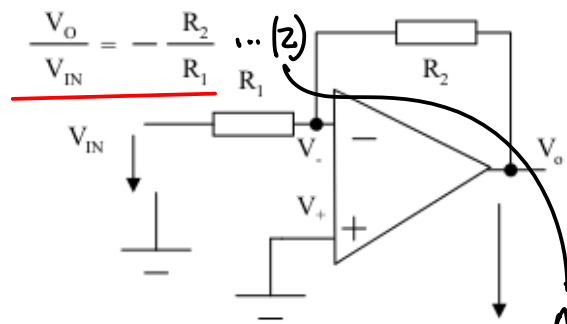




INVERTING

$$A = -\frac{R_2}{R_1}$$

$1 \times 10^{-9} \text{ A}$ or
Smaller
 V_1
 V_2
 $I \ll 8$


Now, consider the design Implementation for 2-Step Process.

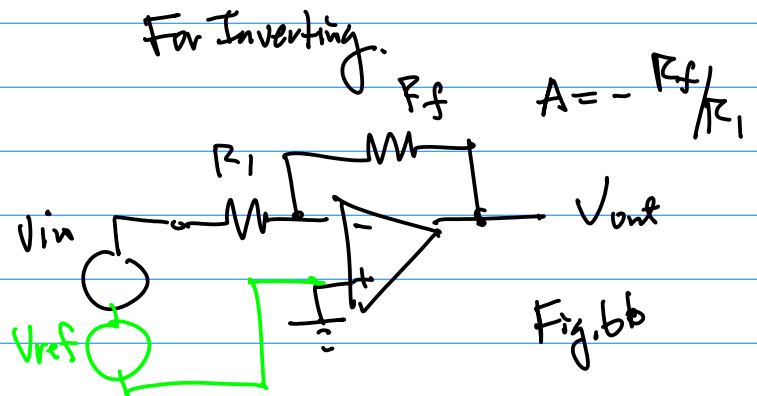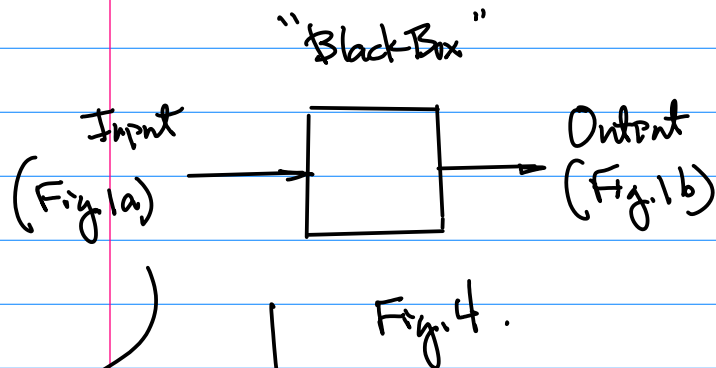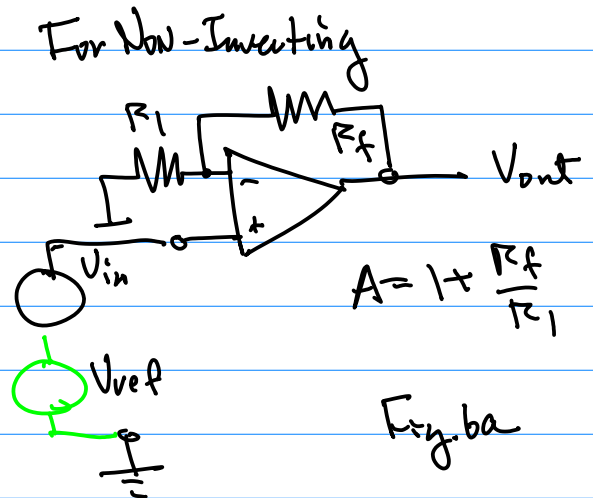Tools $\left\{ \begin{array}{l} \text{Non-Inverting} \sim / \text{Inverting} \sim \\ \text{Linear System: SuperImpose} \\ \text{One Signal (offset)} \\ \text{on to the other} \\ \text{Signal (Input)}. \end{array} \right.$



Linear System: "SuperImpose Signal for Offset"

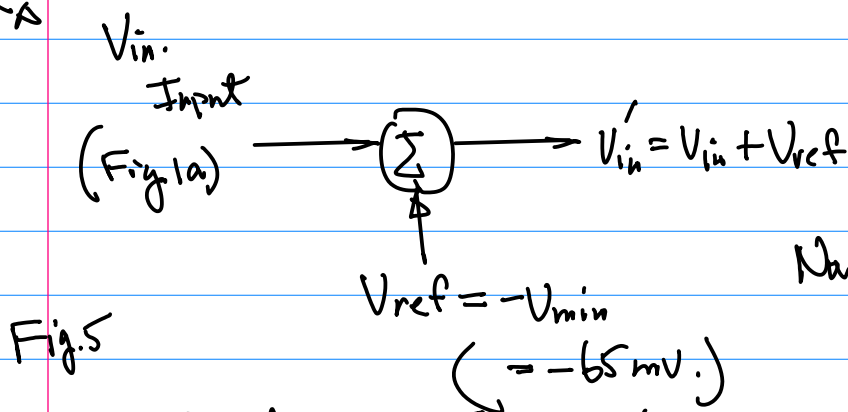Note: Selection of Non- ~ v.s. Inverting Configuration Depends on your design Need. This Design is an illustration of SuperImposing an "offset", e.g. V_{ref} .



In the Circuit Design. Just Connect 2 inputs together.


Now, to Magnify the Signal to match ADC's Dynamic Range. Choose Non-Inverting Configuration (see Fig. 2)

Hence

$$A = 1 + \frac{R_f}{R_1} = 11.58$$

Choose $R_1 = 1 \text{ k}\Omega$
 Solve for $R_f \approx 10.58 \text{ k}\Omega$?
 please verify it!

Stage 1 Stage 2
 Box 1 Box 2

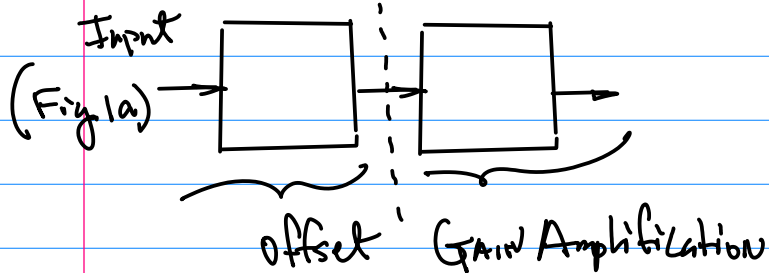


April 12 (Wed).

Note 1. The Last Project Preparation.
 (Requires the Semester End Presentation).


Note 2. Implementation of ADC Unit.

P.O.T. 47K or 470K or Similar.

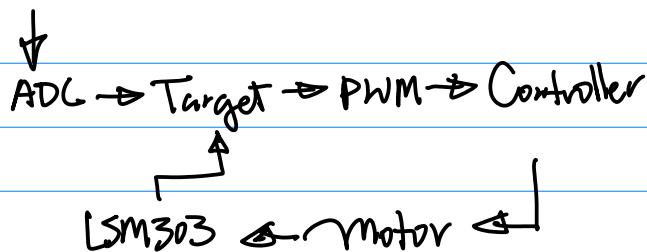

Note 3. ADC Data Validation
 FFT. Power Spectrum.

Note 4. Road Map.

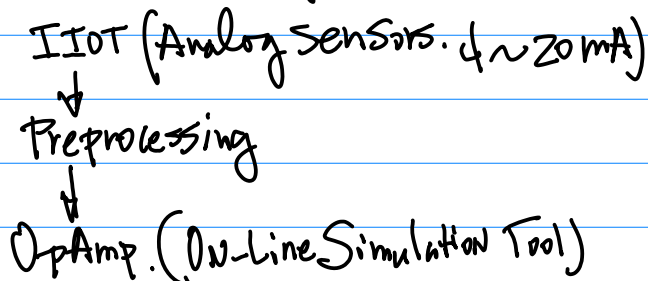

Analog Devices
<https://www.analog.com/ltspice-simulator>

LTspice Information Center

LTspice® is a powerful, fast, and free SPICE simulator software, schematic capture and waveform viewer with enhancements and models for improving the ...

EasyEDA
<https://easyeda.com>


EasyEDA - Online PCB design & circuit simulator

EasyEDA is a free and easy to use circuit design, circuit simulator and in your web browser.

Requirements: To Be Able to Run
 SPICE Simulator.

Free for Download,
 Originated from "Linear"
 A Silicon Valley Company.

Example:

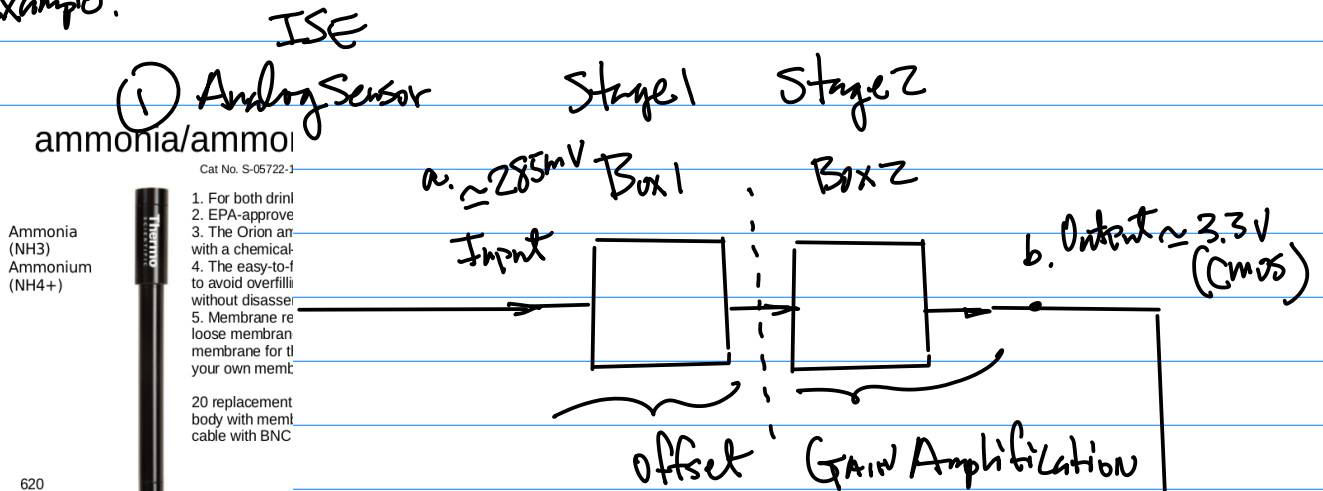

Note: 1° Analog

Sensor—
Signal
Source
Sine
Wave
Signal

2° for min.

Input from the


Sensor. ($\approx 65\text{mV}$)

We want to get

ADC Output = 0.

for Max Input from the Sensor,

We want to get Output: (3.3VDC) 4095
ADC

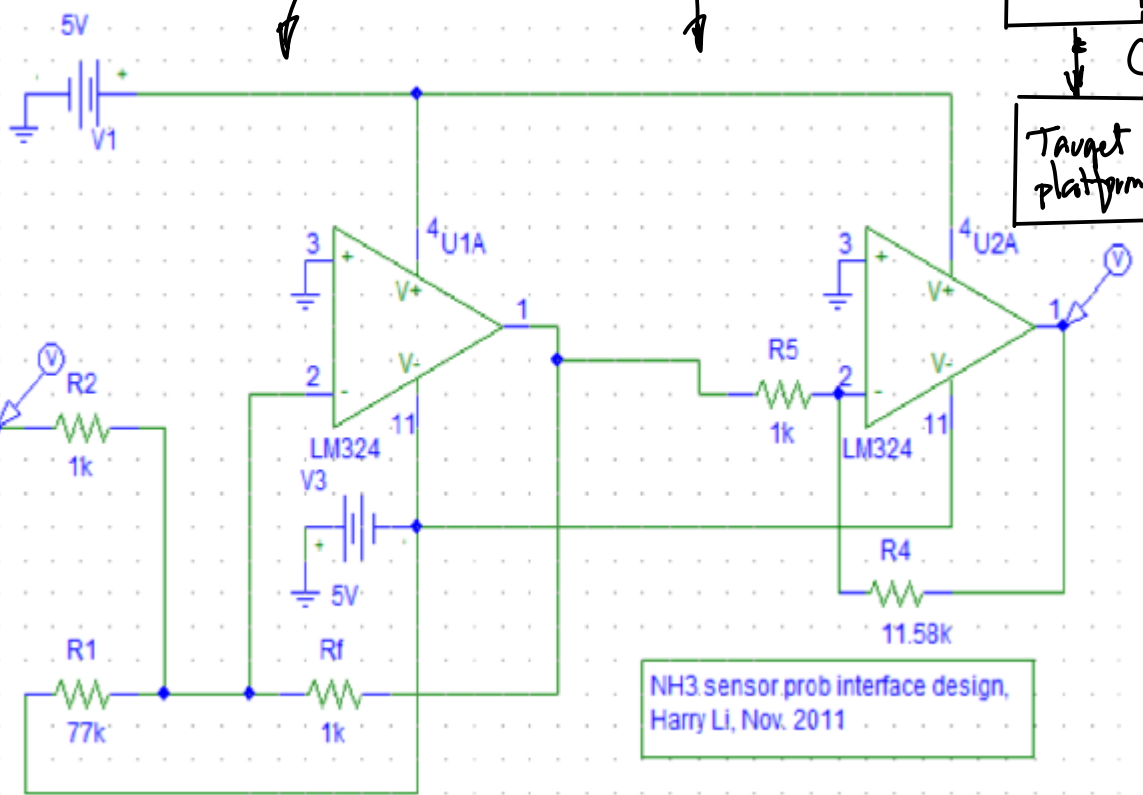

12 bit
ADC
Output
 ≈ 4095

Note: 3. Simulation of the Sensor Output as the input to the pre-processing circuit.

