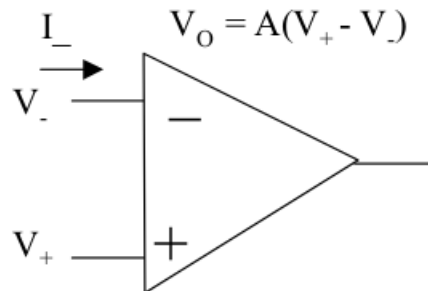




OpAmp Device As a Buffering Stage

Both Analog and Digital Circuit




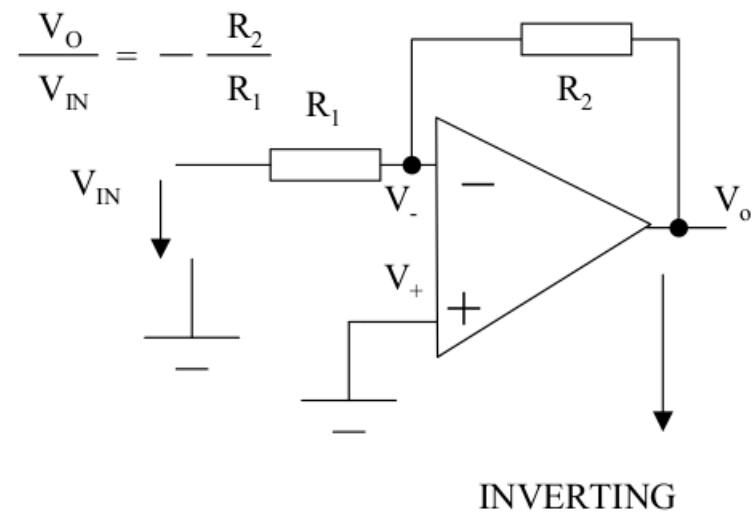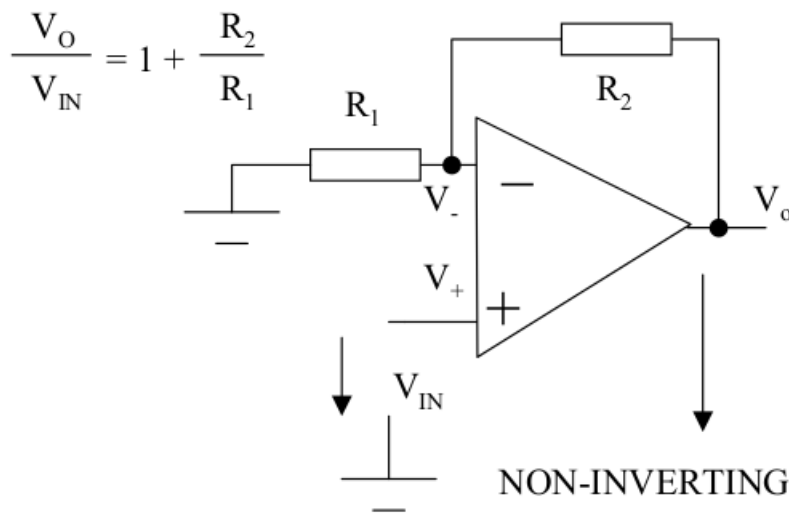(1) To protect the previous stage's output signal, which is the input to the next stage, while sampling/connecting the signal to its next stage logic circuit. (2) Unit gain non-inverting OpAmp configuration is an excellent choice.

Ideal OpAmp Properties: (1) very large gain, $A \gg M$; (2) draws very little current, $I_- \sim 0$, e.g., very high impedance; (3) $V_O = A(V_+ - V_-)$ is finite range, which leads to $V_+ = V_-$.




Circuit Design for NH3 Sensor

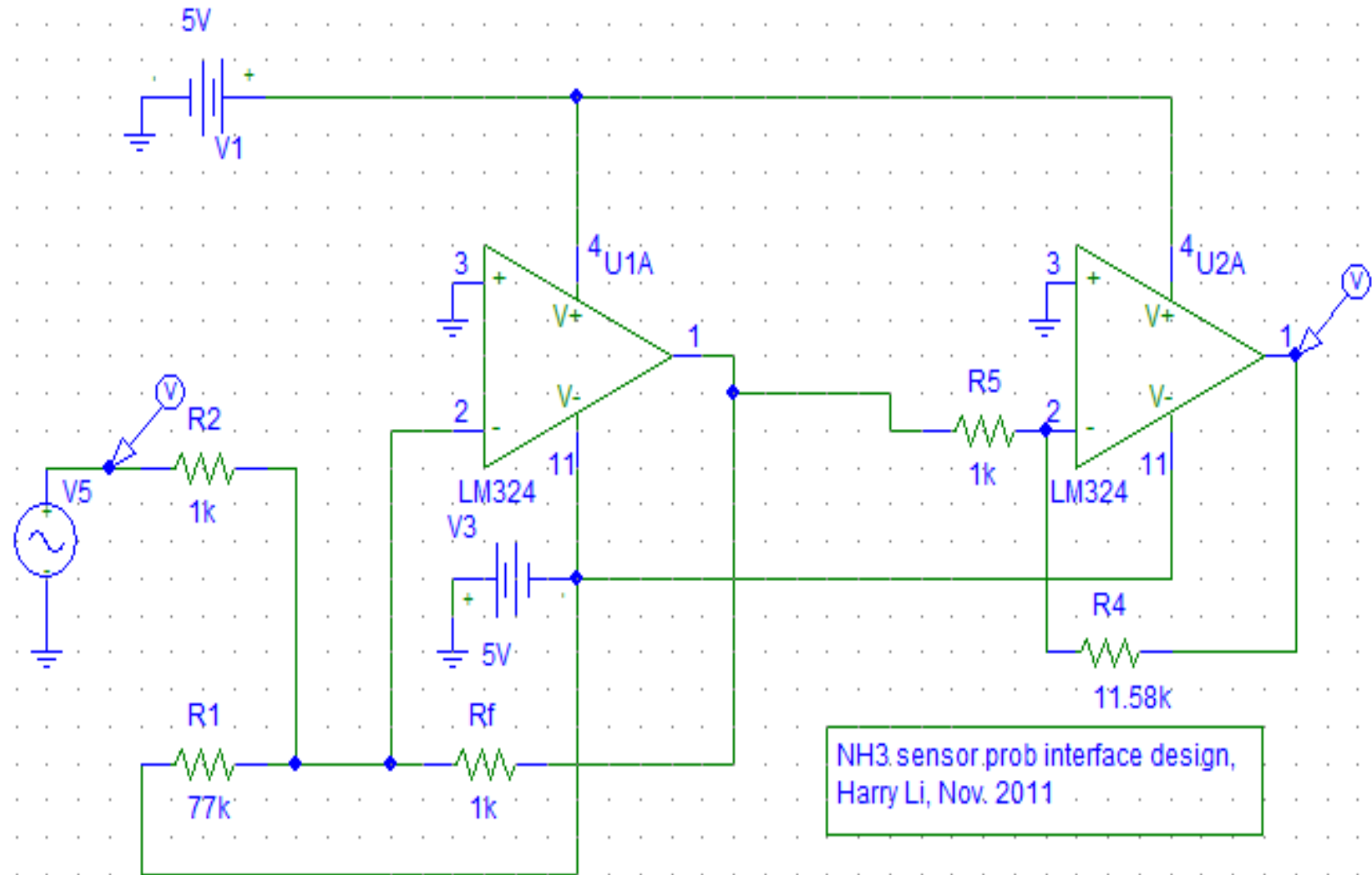


Simulation Result

The output:
3.3V

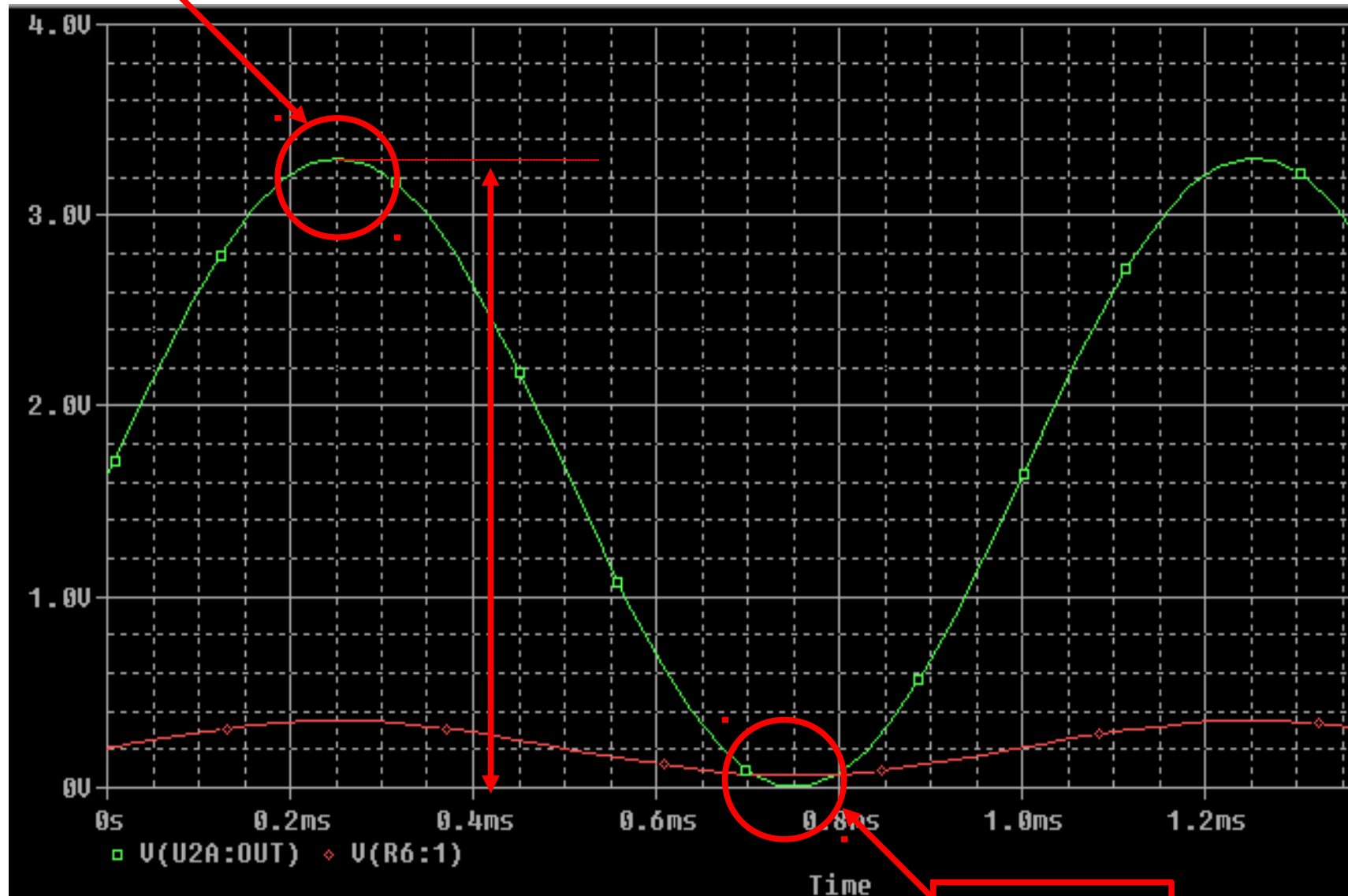


The input
offset 65mV

Arithmetic With OpAmps

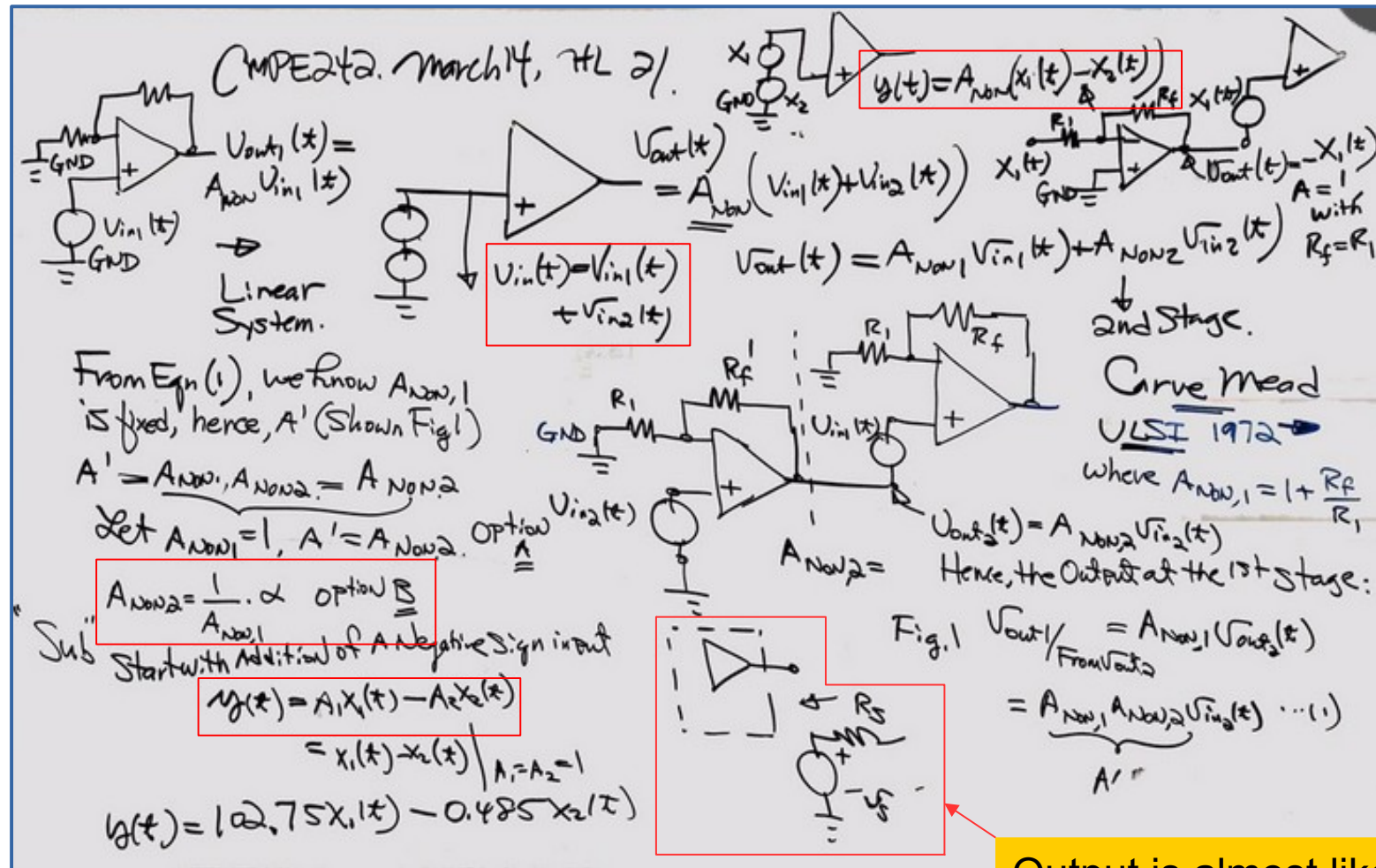

Reference: Some Of My Work

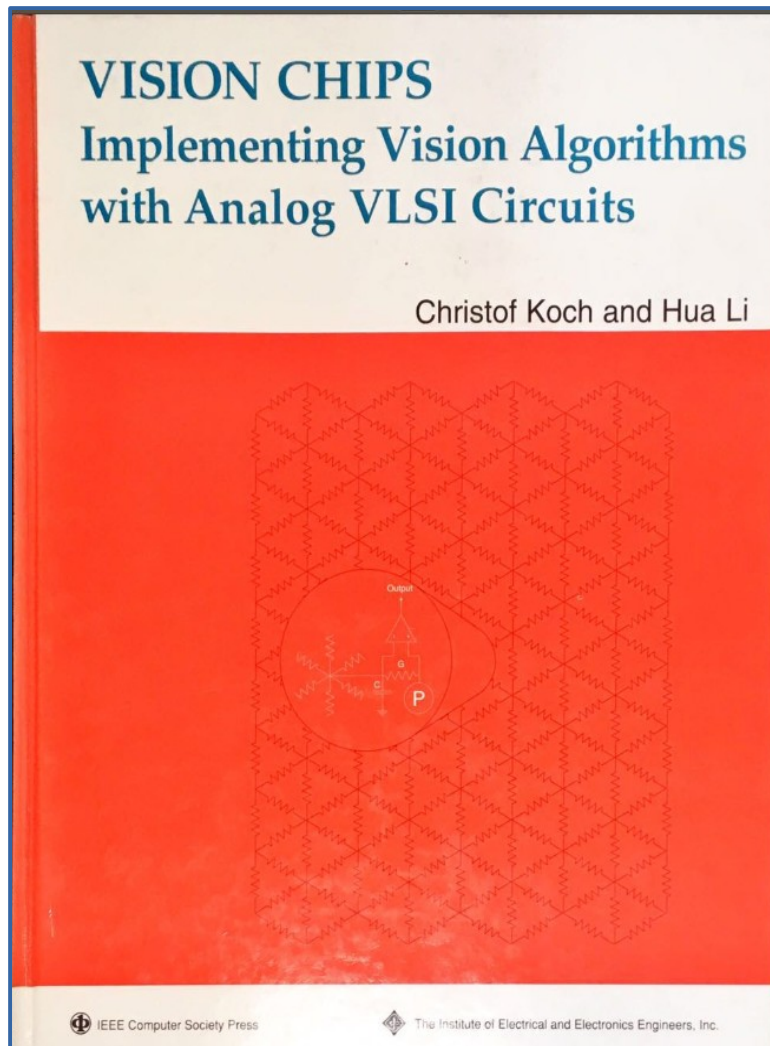

Silicon Neuron idea pioneered by Carver Mead, who is credited as the inventor of standardized VLSI (Very Large Scale Integrated Electronic Circuits) design, has proposed building a silicon neuron machine, e.g., silicon brain. Inspired by his work, I have ventured in the Analog VLSI technique to build Vision Chips, and did edited book with Christoff Koch. Carver Mead and our book was primary reference for the IEEE Spectrum cover story, Artificial Eye.

